

Blizzard Bag Day #3

Justify answers, showing work or explaining.

1. What is the current and voltage across each resistor if a 9 V battery is attached?

